


LED Display

Prof. Betty Lise Anderson





Here's what you're going to build

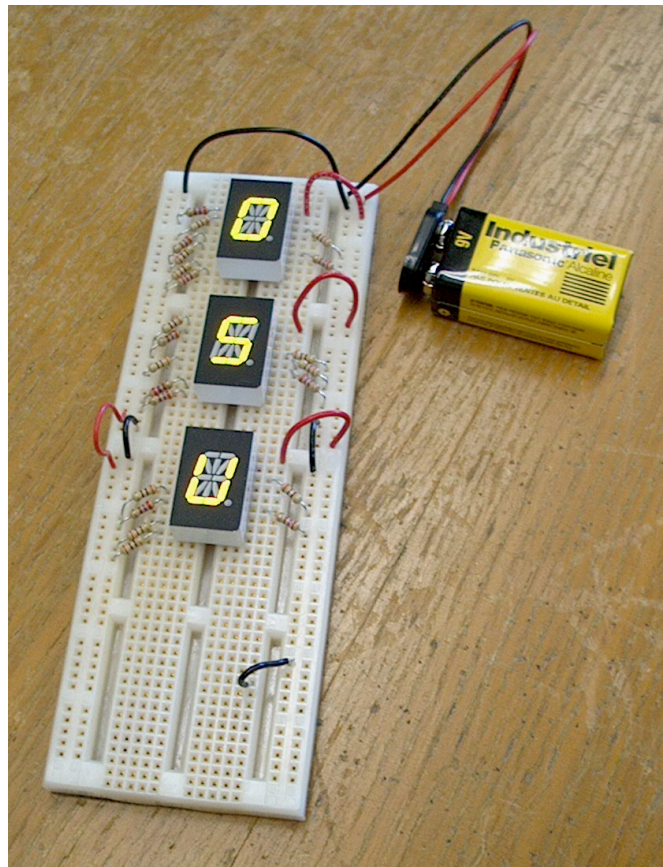



Need to learn some things


- How to read an electrical schematic
- What parts we're using
- How design the display
- How to build the display



Reading Schematics:

What's this?

- Battery

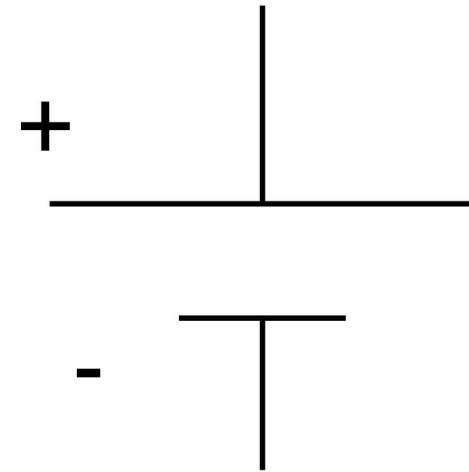



How about this?


- Resistor






What's this?

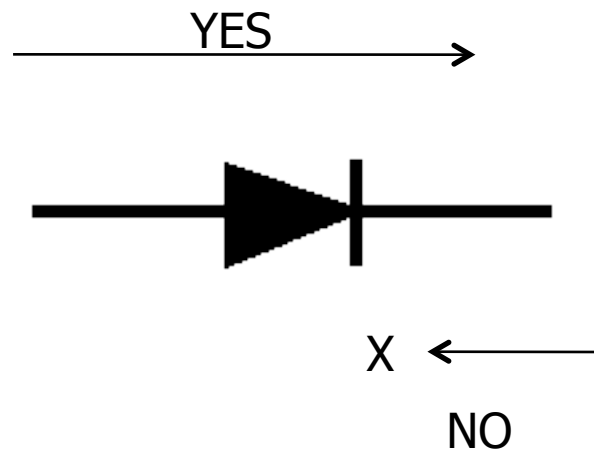- Diode
 - Lets current flow one direction but not the other






Will current flow?

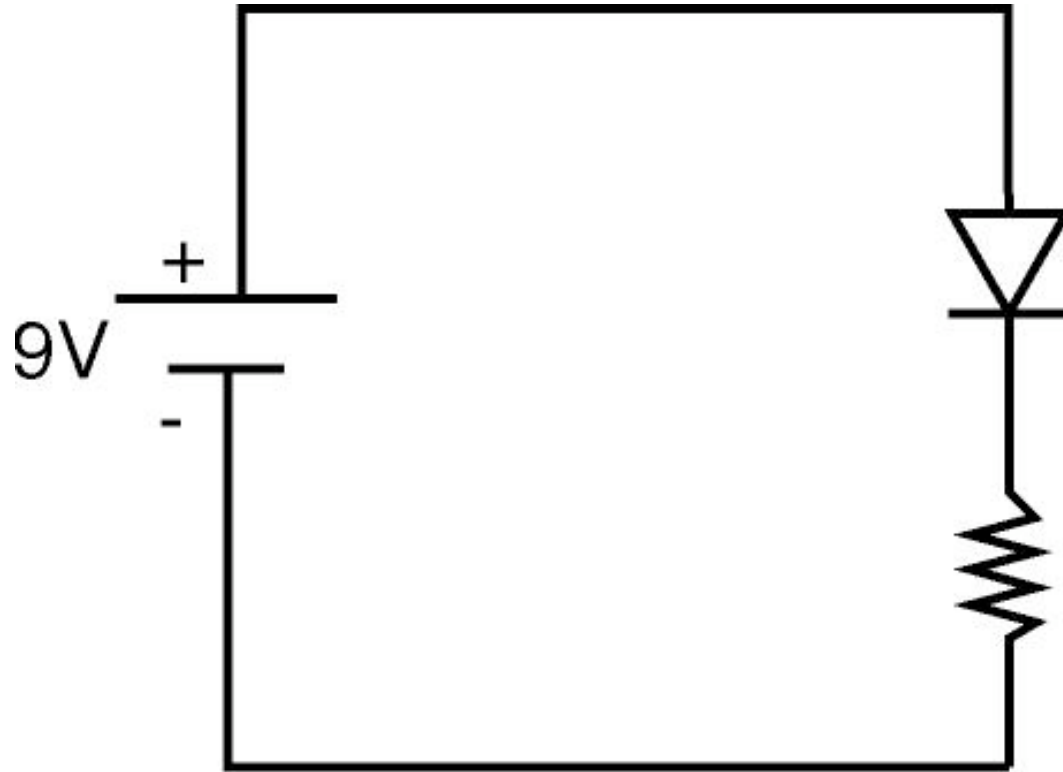




How about here?

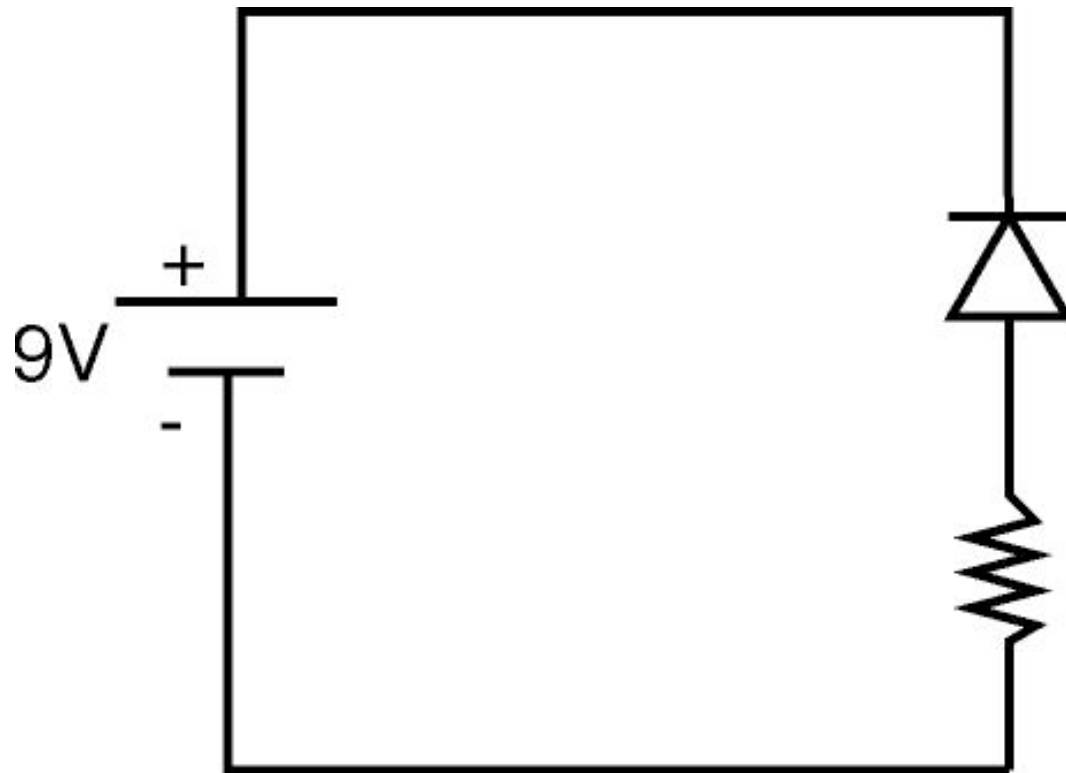




And here?

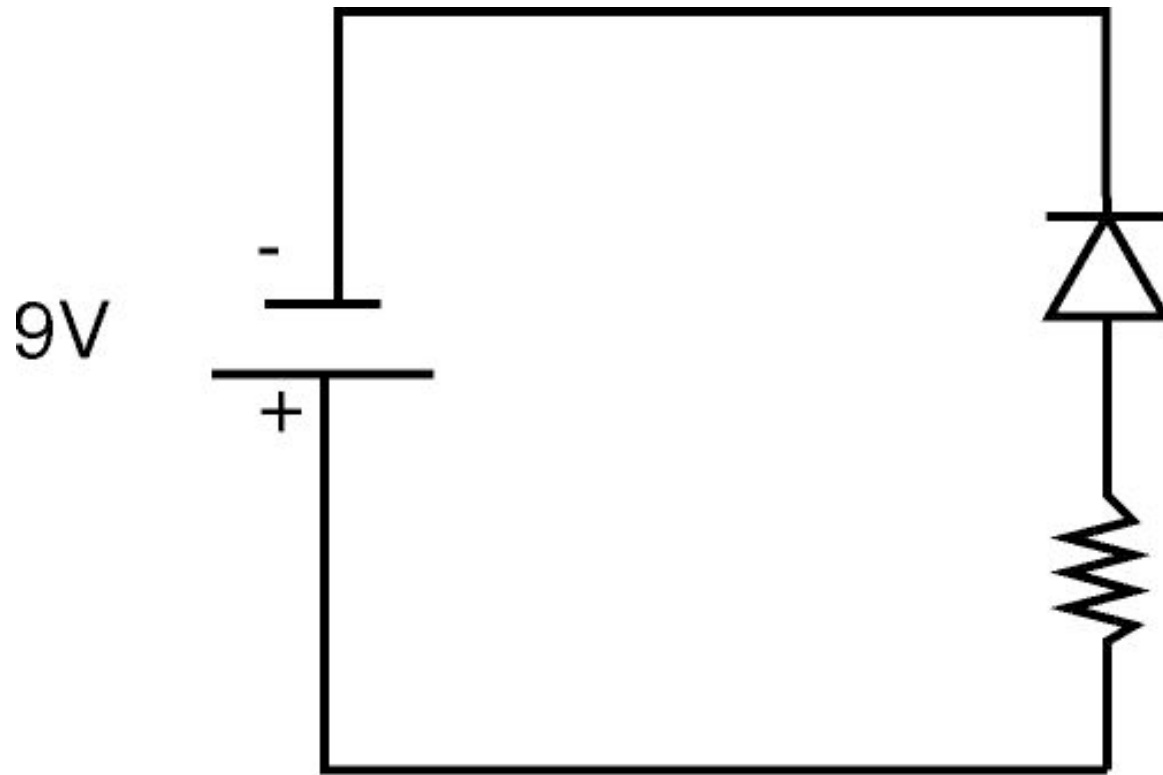

Let's take a look at the components

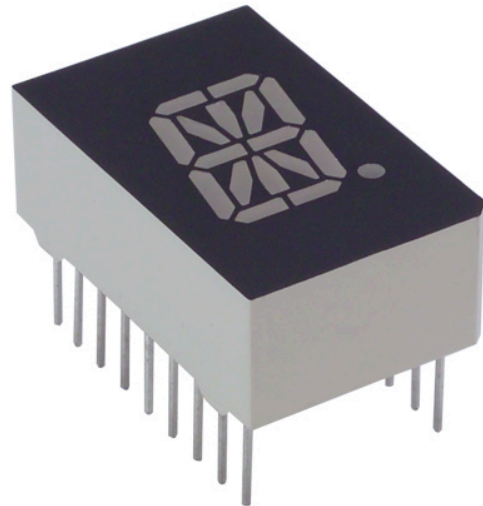

- 16-segment alphanumeric display
 - Green, yellow, or red
- 18-pin package
- There is one LED inside for each segment



How to read the data sheet

- This page is general propaganda

LITEON LITE-ON ELECTRONICS, INC.
Property of Lite-On Only

FEATURES

- *0.5-INCH (12.7-mm) DIGIT HEIGHT.
- *CONTINUOUS UNIFORM SEGMENTS.
- *LOW POWER REQUIREMENT.
- *EXCELLENT CHARACTERS APPEARANCE.
- *HIGH BRIGHTNESS & HIGH CONTRAST.
- *WIDE VIEWING ANGLE.
- *SOLID STATE RELIABILITY.
- *CATEGORIZED FOR LUMINOUS INTENSITY.

DESCRIPTION

The LTP-587HR is a 0.5-inch (12.7-mm) height 16-segment single digit alphanumeric display. This device utilizes high efficiency red LED chips, which are made from GaAsP on GaP substrate, and has a red face and red segments.


DEVICE

PART NO.	DESCRIPTION
HI-EFF. RED	Common Anode,
LTP-587HR	Rt. Hand decimal



Next is dimensinos

PACKAGE DIMENSIONS

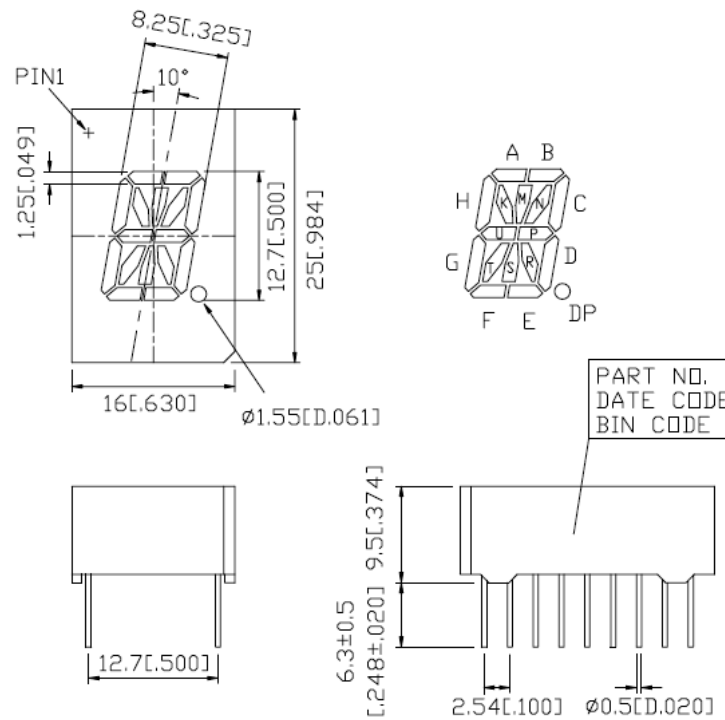


NOTES: All dimensions are in millimeters. Tolerances are ± 0.25 -mm (0.01") unless otherwise noted.



Ah hah! What's inside

INTERNAL CIRCUIT DIAGRAM

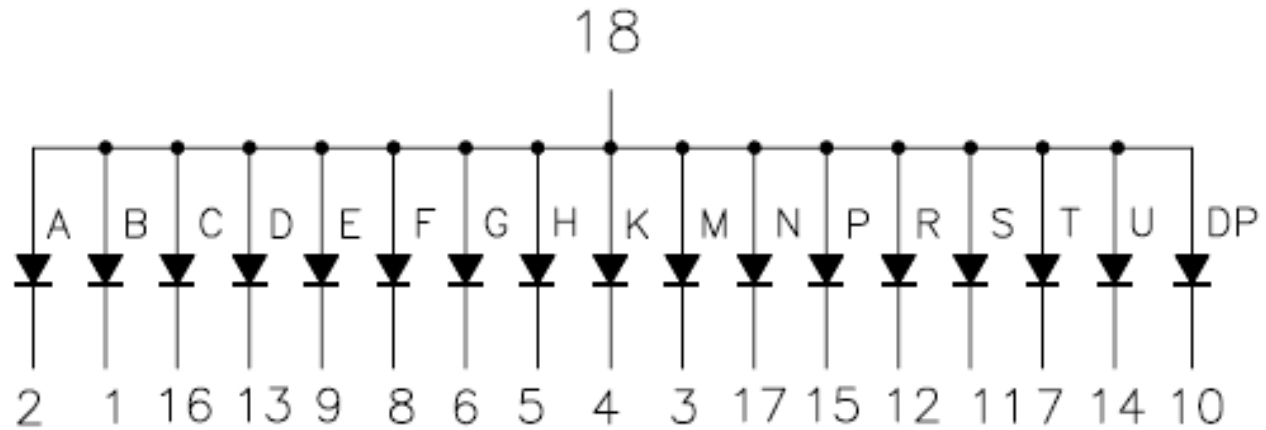




This is called the pinout

PIN CONNECTION

No.	CONNECTION
1	CATHODE B
2	CATHODE A
3	CATHODE M
4	CATHODE K
5	CATHODE H
6	CATHODE G
7	CATHODE T
8	CATHODE F
9	CATHODE E
10	CATHODE D.P.
11	CATHODE S
12	CATHODE R
13	CATHODE D
14	CATHODE U
15	CATHODE P
16	CATHODE C
17	CATHODE N
18	COMMON ANODE

TOP VIEW

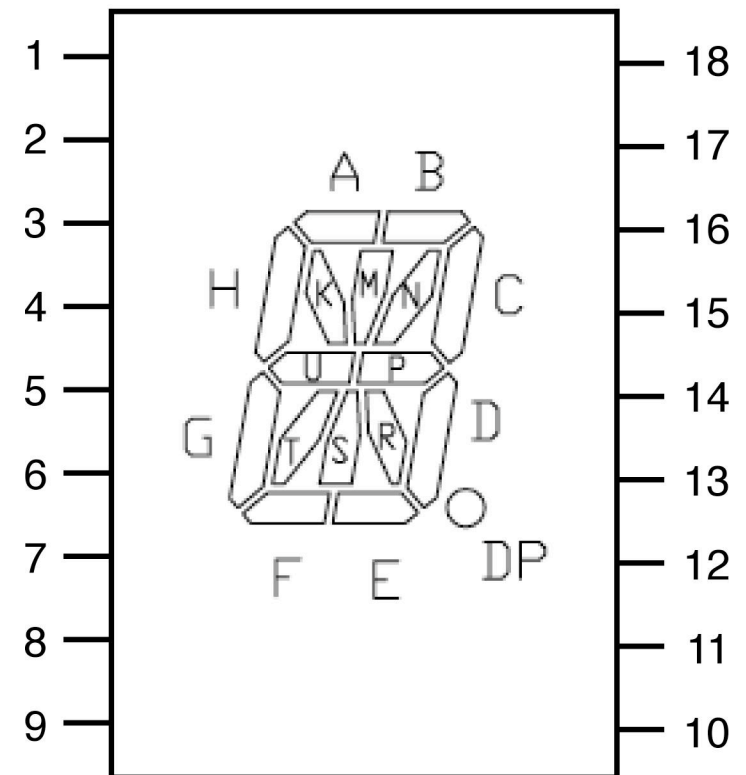



Absolute maximum ratings

ABSOLUTE MAXIMUM RATING AT $T_a=25^{\circ}\text{C}$

PARAMETER	MAXIMUM RATING	UNIT
Power Dissipation Per Segment	75	mW
Peak Forward Current Per Segment (1/10 Duty Cycle, 0.1ms Pulse Width)	100	mA
Continuous Forward Current Per Segment	25	mA
Derating Linear From 25°C Per Segment	0.33	mA/ $^{\circ}\text{C}$
Reverse Voltage Per Segment	5	V
Operating Temperature Range	-35°C to $+85^{\circ}\text{C}$	
Storage Temperature Range	-35°C to $+85^{\circ}\text{C}$	
Solder Temperature 1/16 inch Below Seating Plane for 3 Seconds at 260°C		



Electro-optical characteristics

ELECTRICAL / OPTICAL CHARACTERISTICS AT $T_a=25^\circ\text{C}$

PARAMETER	SYMBOL	MIN.	TYP.	MAX.	UNIT	TEST CONDITION
Average Luminous Intensity	I_v	800	2200		μcd	$I_F=10\text{mA}$
Peak Emission Wavelength	λ_p		635		nm	$I_F=20\text{mA}$
Spectral Line Half-Width	$\Delta\lambda$		40		nm	$I_F=20\text{mA}$
Dominant Wavelength	λ_d		623		nm	$I_F=20\text{mA}$
Forward Voltage, Per Segment	V_F		2.0	2.6	V	$I_F=20\text{mA}$
Reverse Current, Per Segment	I_R			100	μA	$V_R=5\text{V}$
Luminous Intensity Matching Ratio	$I_v\text{-m}$			2:1		$I_F=10\text{mA}$



Additional information

TYPICAL ELECTRICAL / OPTICAL CHARACTERISTIC CURVES

(25°C Ambient Temperature Unless Otherwise Noted)

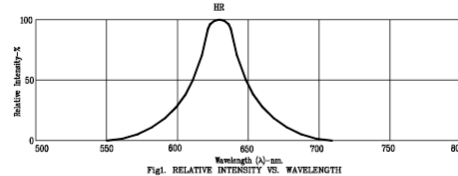


Fig.1. RELATIVE INTENSITY VS. WAVELENGTH

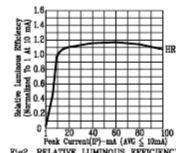


Fig.2. RELATIVE LUMINOUS EFFICIENCY (LUMINOUS INTENSITY PER UNIT CURRENT) VS. PEAK CURRENT (REFRESH RATE 1KHz)

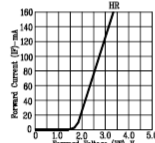


Fig.3. FORWARD CURRENT VS. FORWARD VOLTAGE

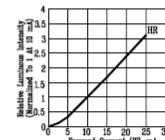


Fig.4. RELATIVE LUMINOUS INTENSITY VS. FORWARD CURRENT

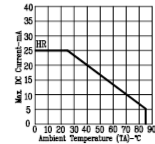


Fig.5. MAX. ALLOWABLE DC CURRENT VS. AMBIENT TEMPERATURE


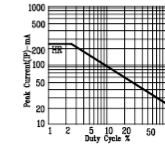


Fig.6. MAX. PEAK CURRENT VS. DUTY CYCLE % (REFRESH RATE 1KHz)

NOTE: HR=III-EFF.RED

What value of resistor?

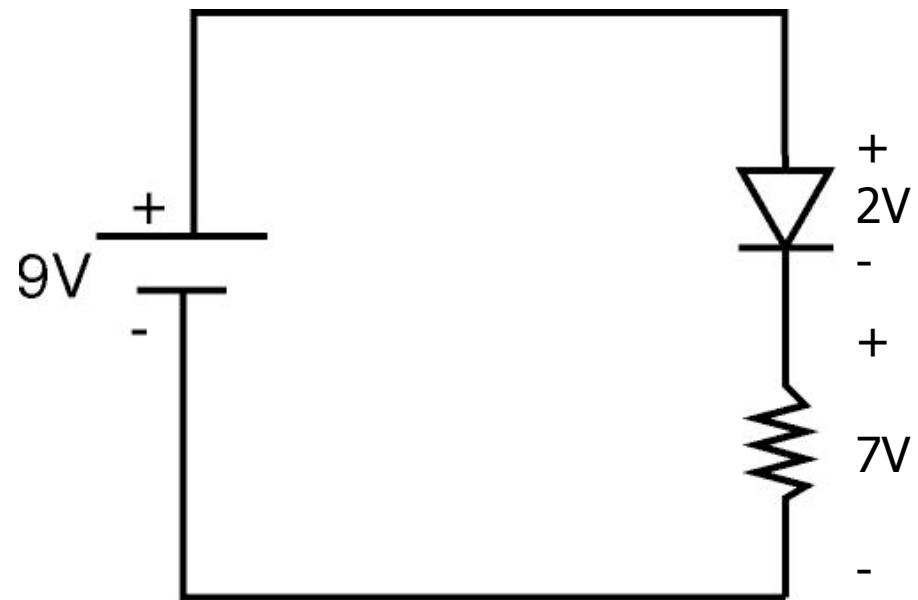
- What is voltage across the diode?
 - Hint: look at electro-optical characteristics
- How much is left to go across the resistor?





$V=IR$

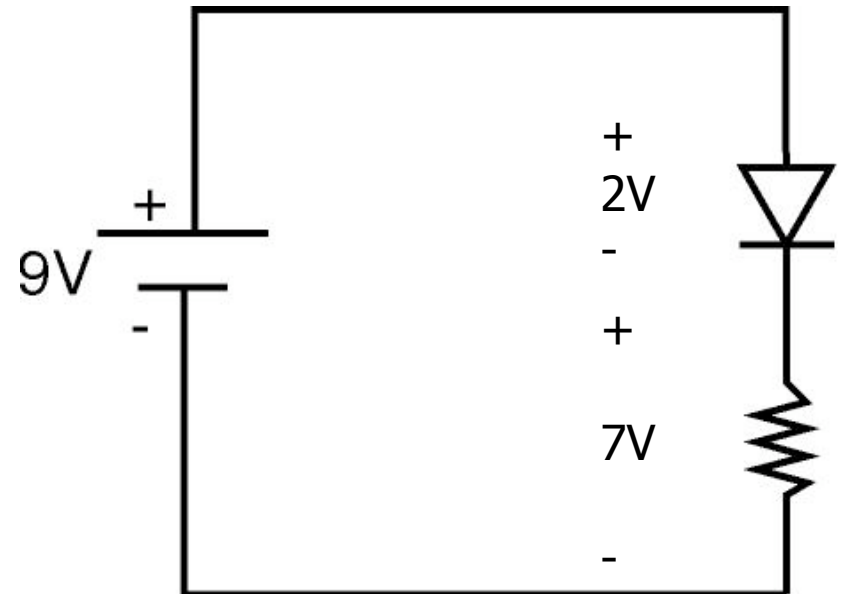
- I = current
- R = resistance
- Don't exceed 25 mA through diode
 - see absolute maximum ratings)
- What are tradeoffs in choosing current?





So, what will you choose?

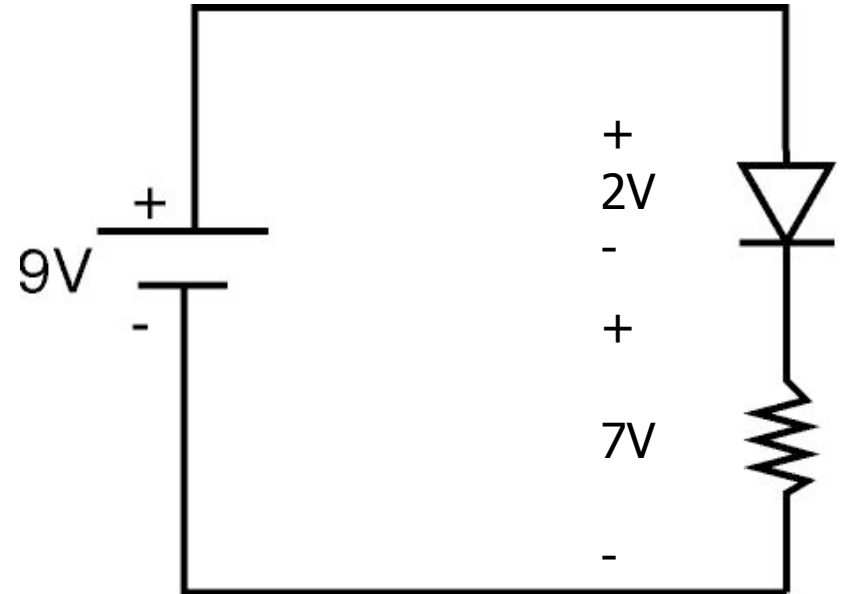- $R = V/I$
- Example:
 - $V = 7V$
 - Choose $I = 20 \text{ mA}$
 - 0.020 Amps
 - $R = 7/0.02 = 350 \text{ Ohms}$
 - We don't have that
 - But we have something close





So here's what you'll build




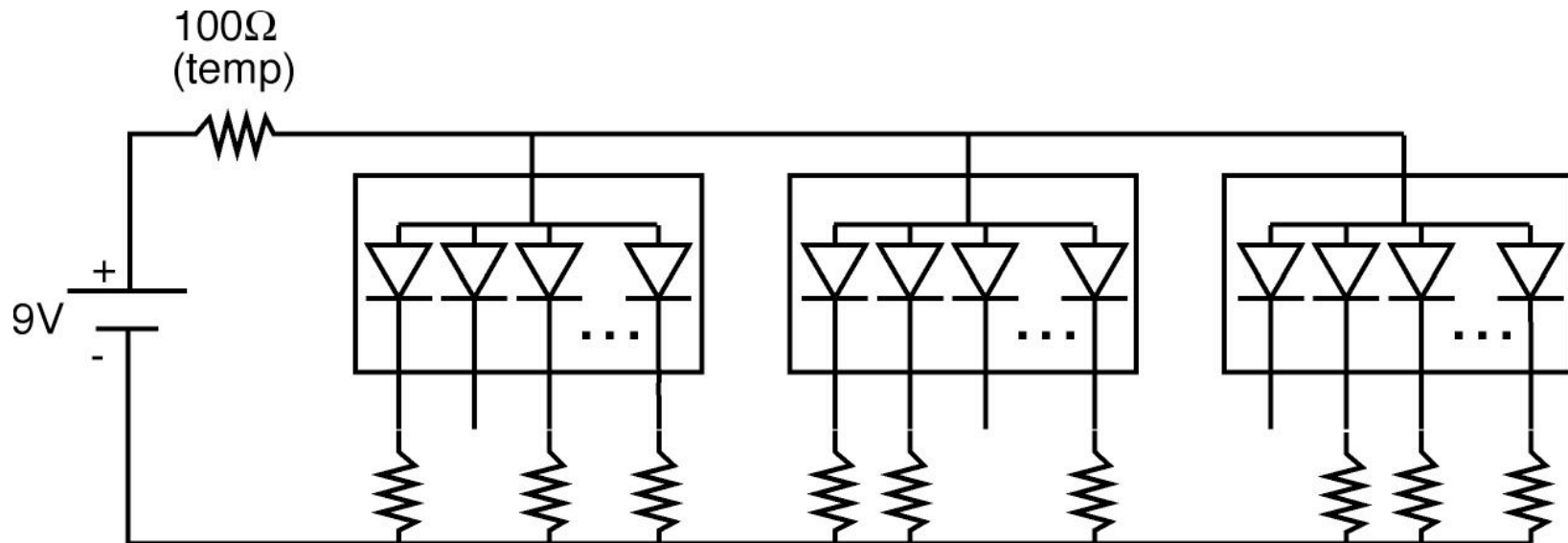
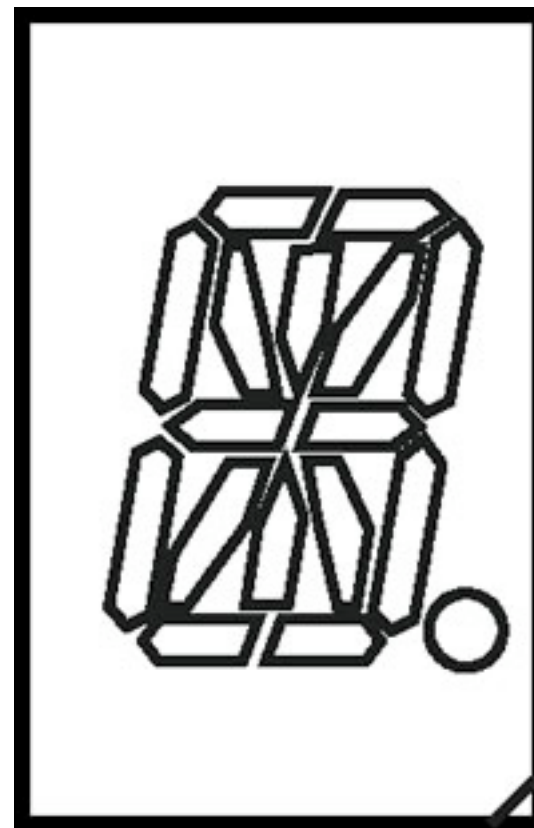


Figure out what to write

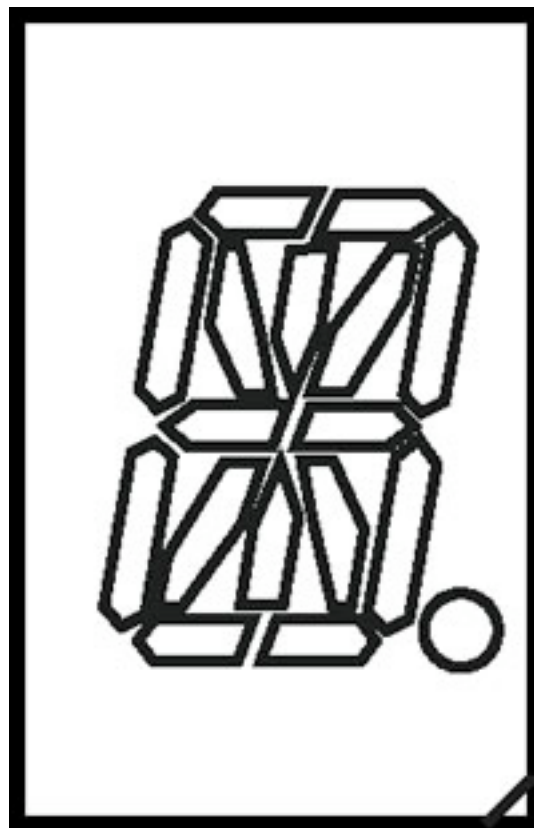

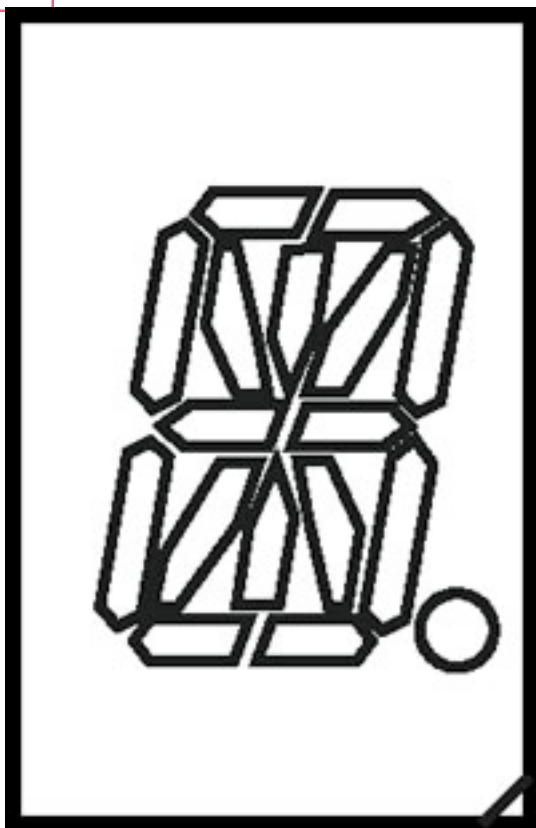


The breadboard

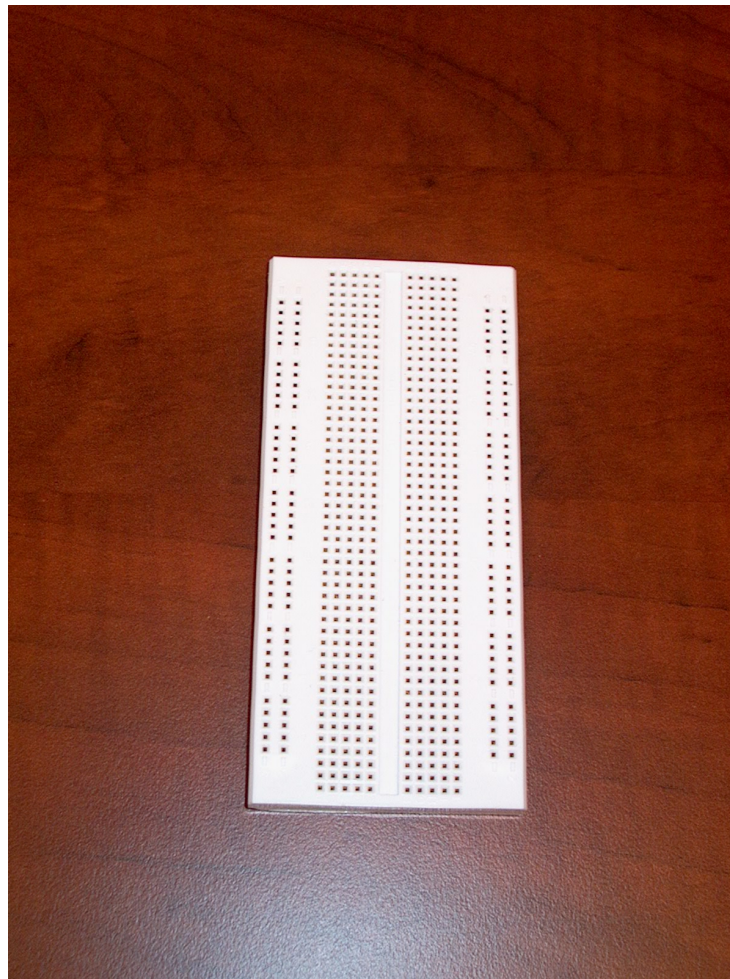




The buses

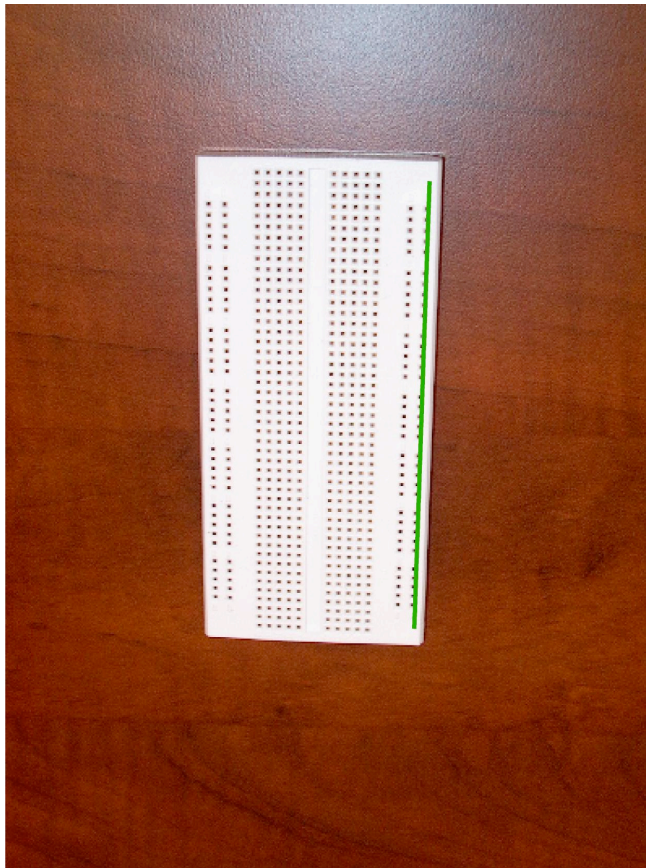


Every hole along this green line is electrically connected

There are four buses you can use

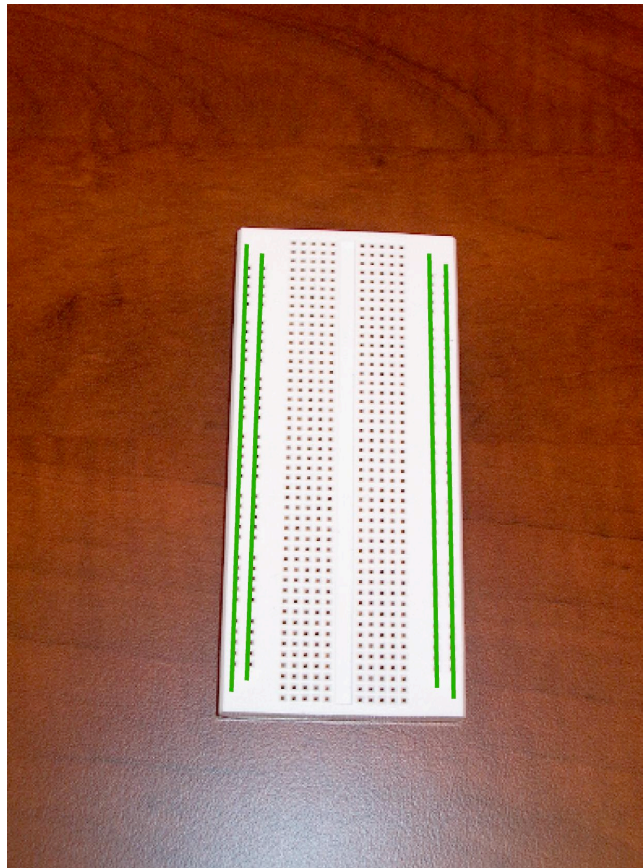




All rows connected too

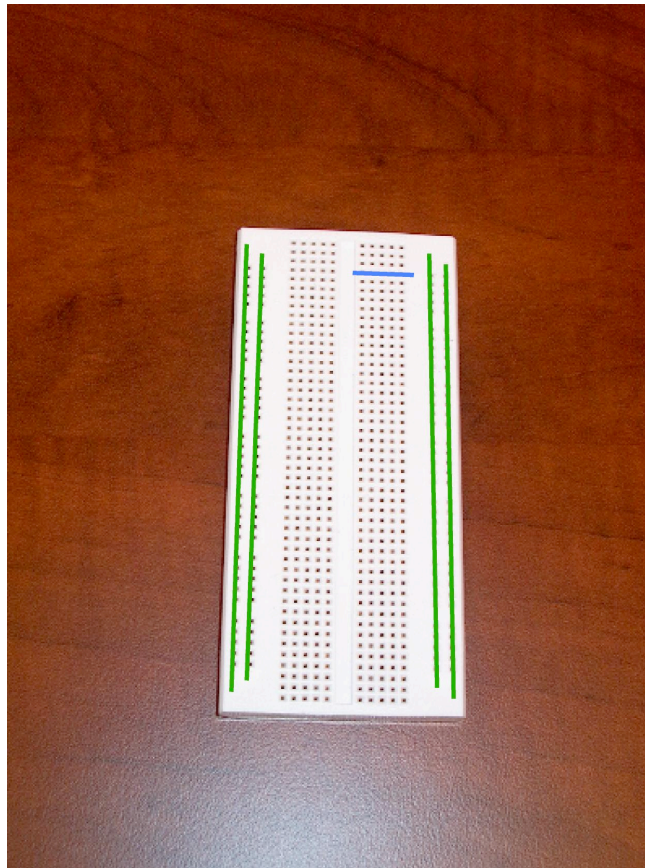

To connect to your devices

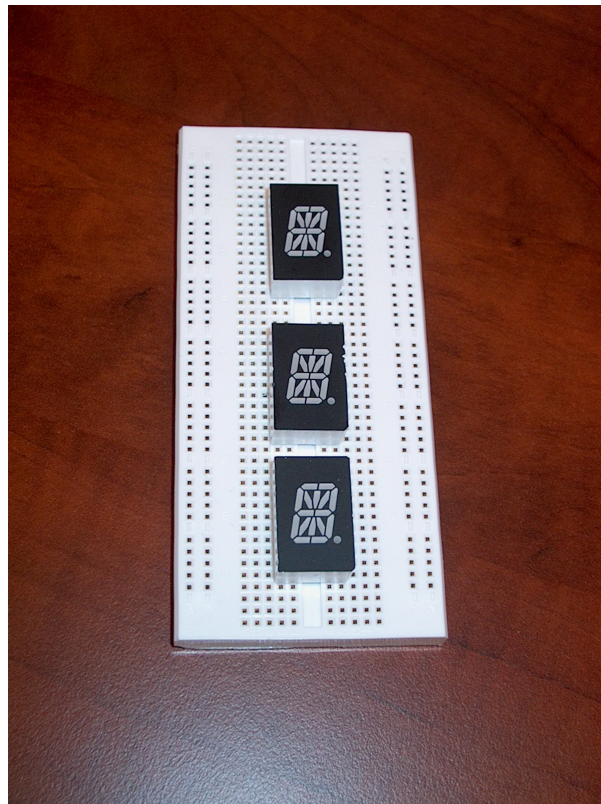


- Recommend putting displays across center channel



To make connections

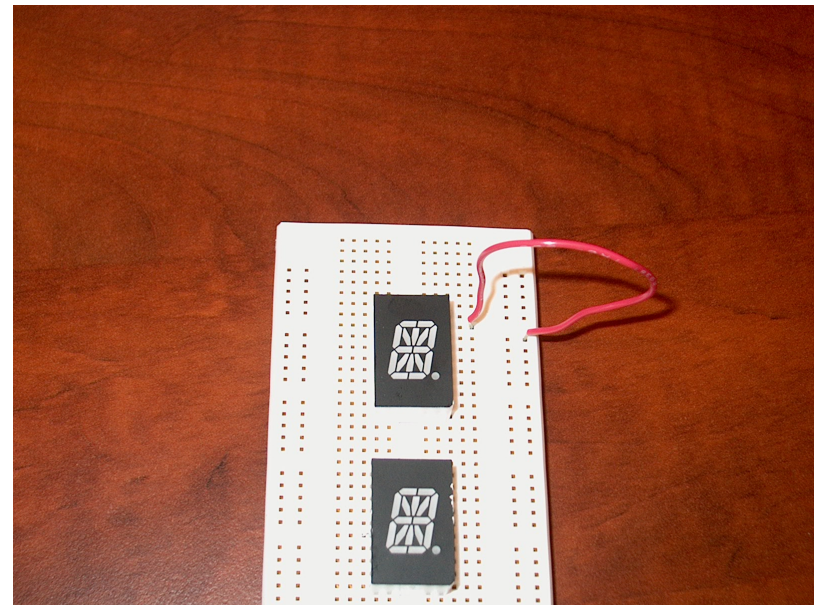
- One end of wire is connected to the bus
 - And anything else connected there
- Other end is connected to one pin






Now, look at circuit diagram

- Need to make these connections

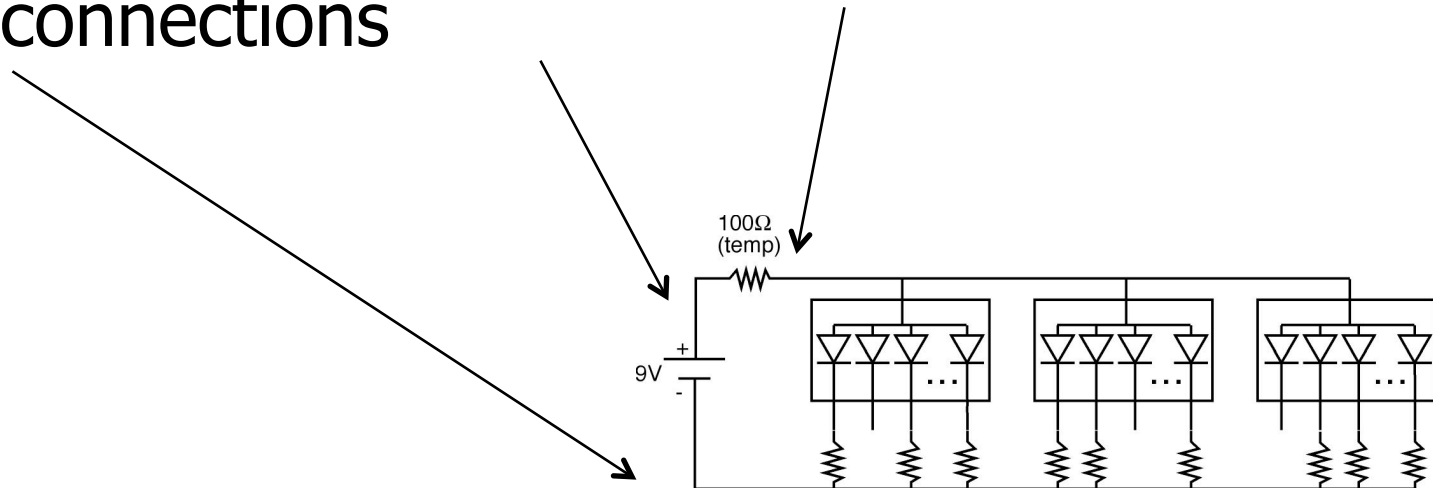


Negative bus and safety resistor

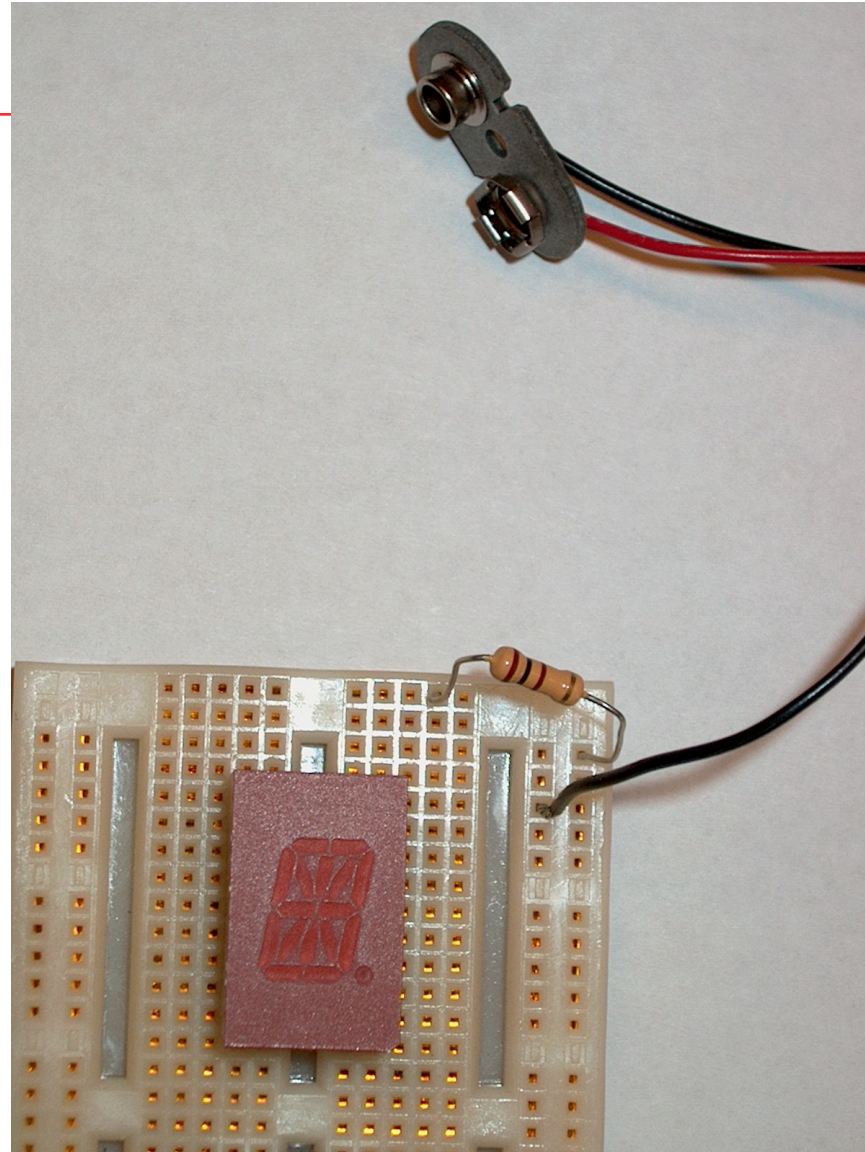




Connect positive

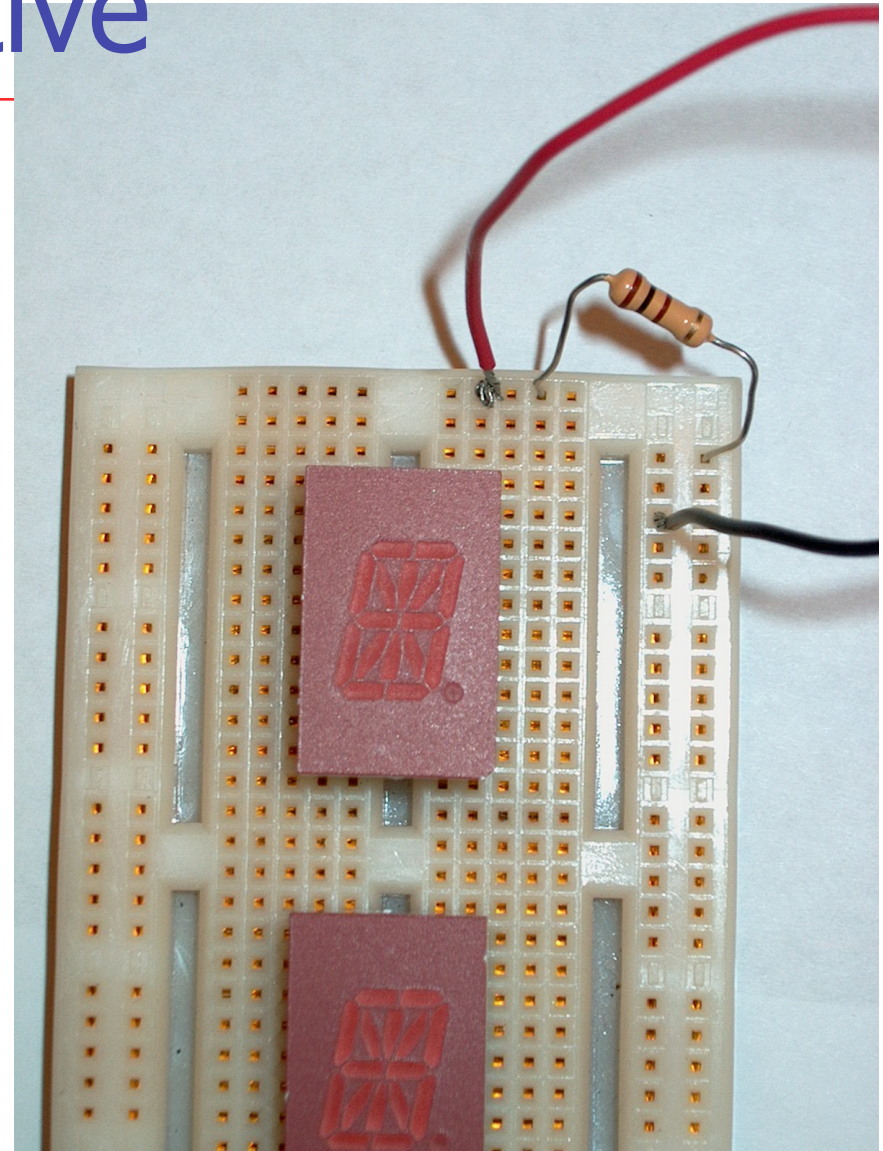



Now, look at circuit diagram

- Need to make this connections

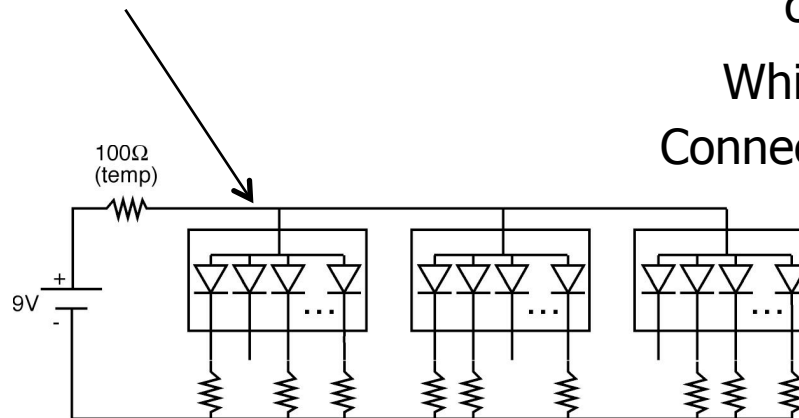


What pin is this on the display?

All anodes connected to a common point at this pin


Which pin is the common anode?

Connect pin 18 to the positive bus

Connect common anode to positive bus

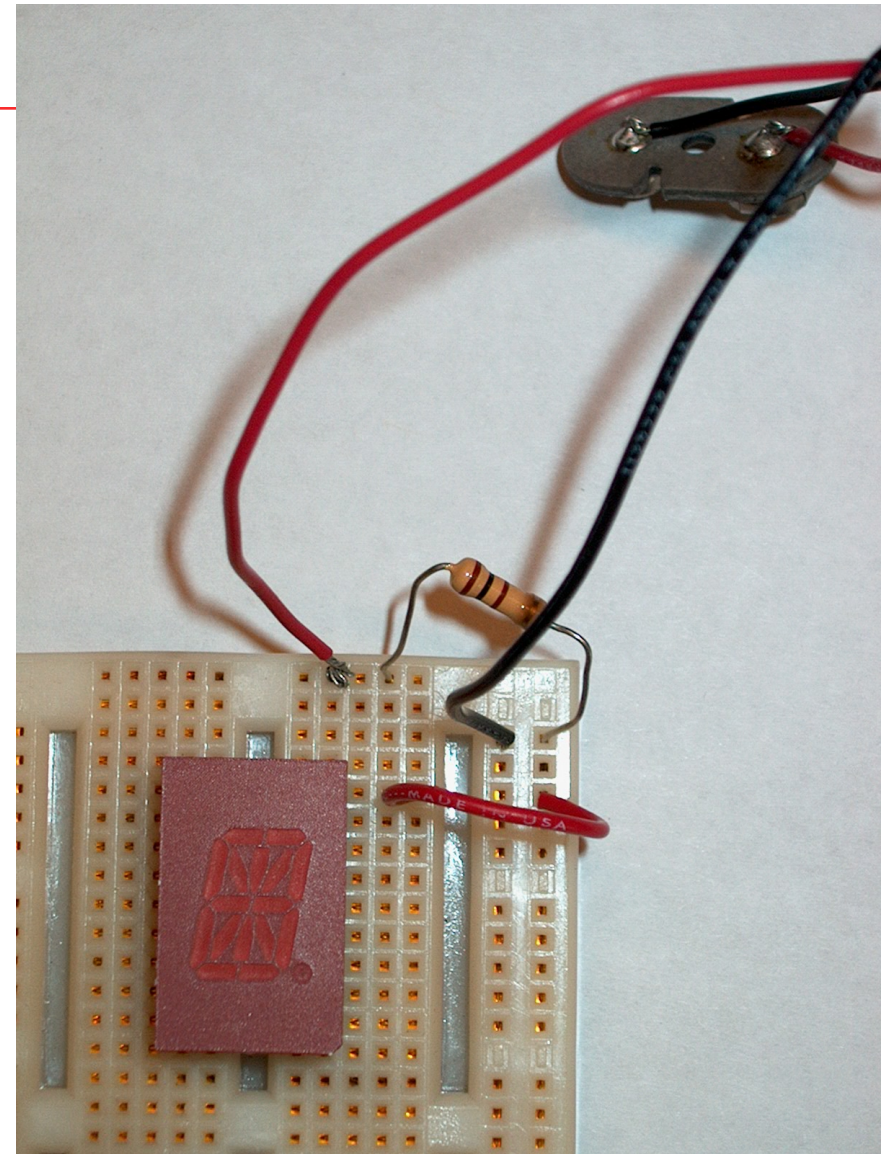


Another negative bus will come in handy

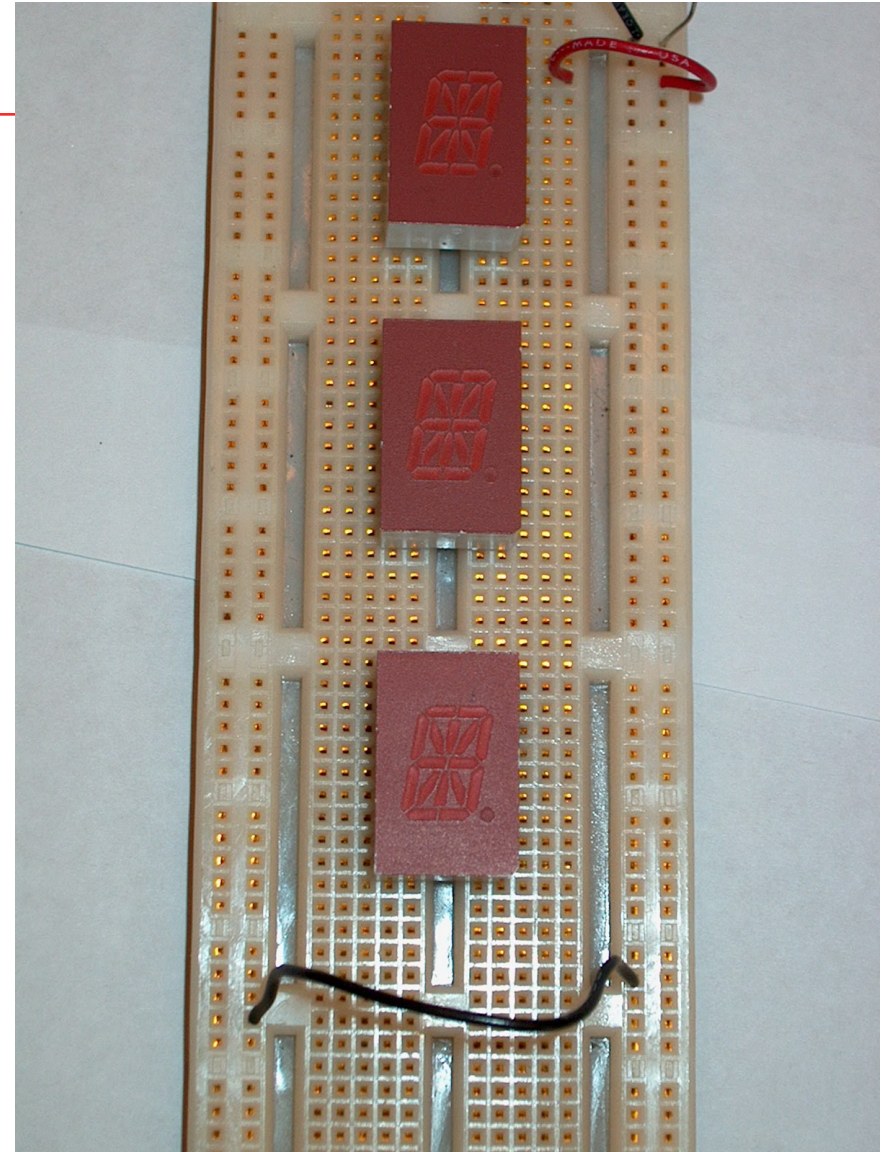




Next, connect cathodes

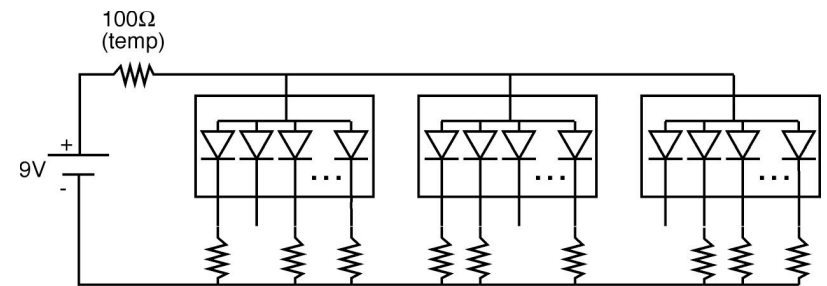- One resistor for every segment you want to light?
- Where do you connect them?





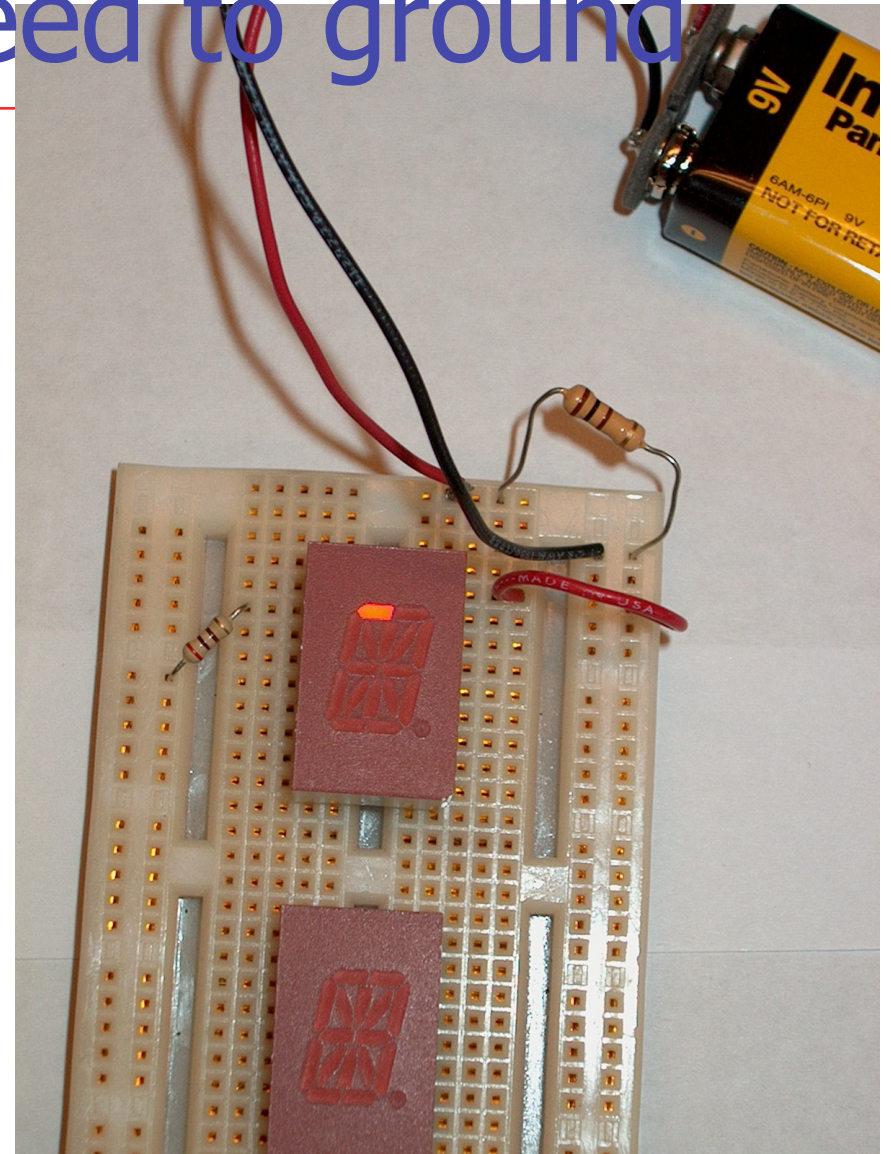Connect resistor for every cathode you need to ground





OK, once it's working

- Repeat for every other segment
- Once done, remove safety resistor